Name _____ Period _____

Physics – Electric Circuits Quiz 1

1. Draw a circuit diagram symbol for:

   a) a cell

   b) a light bulb

2. Draw a section of a circuit that has:

   a) 3 cells in series

   b) 3 cells in parallel

   c) 3 bulbs in series

   d) 3 bulbs in parallel

3. Describe the function of each in the circuit

   a) cell

   b) bulbs

   c) wires